

## Digital clock used components :

1 – 6 \* 7448 ic

2 – 8 \* 7490 ic

3 – 200 male to male wire

4 – 555 timer










5- 2 \* 10 micro farad capacitor

6- 4 \* BreadBoard


7- 6 \* 7 segment cathode display

8- power supply

9 – 2 10k ohm resistors

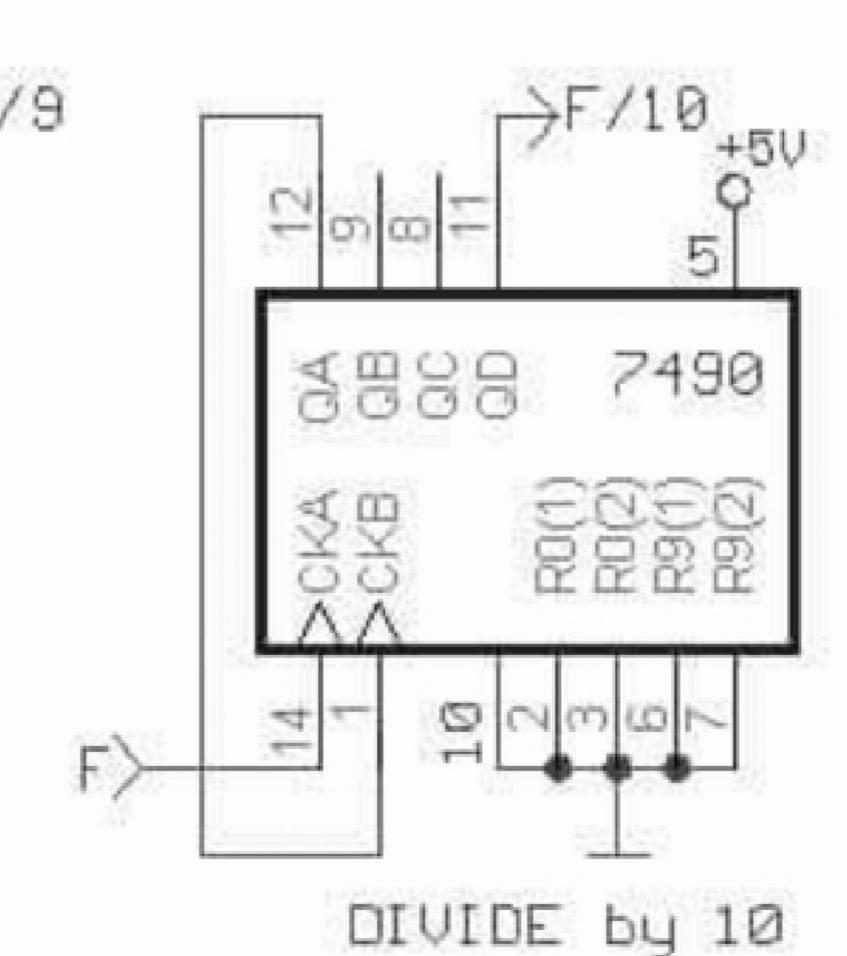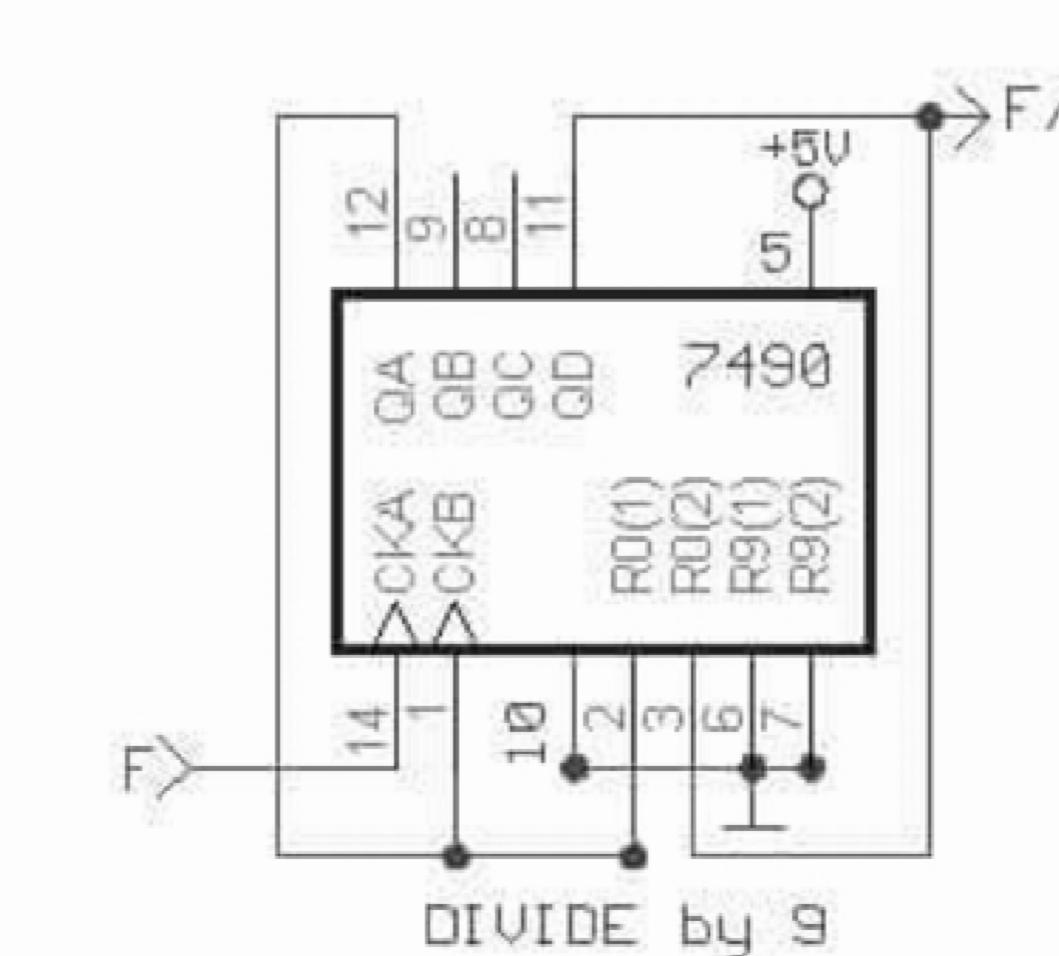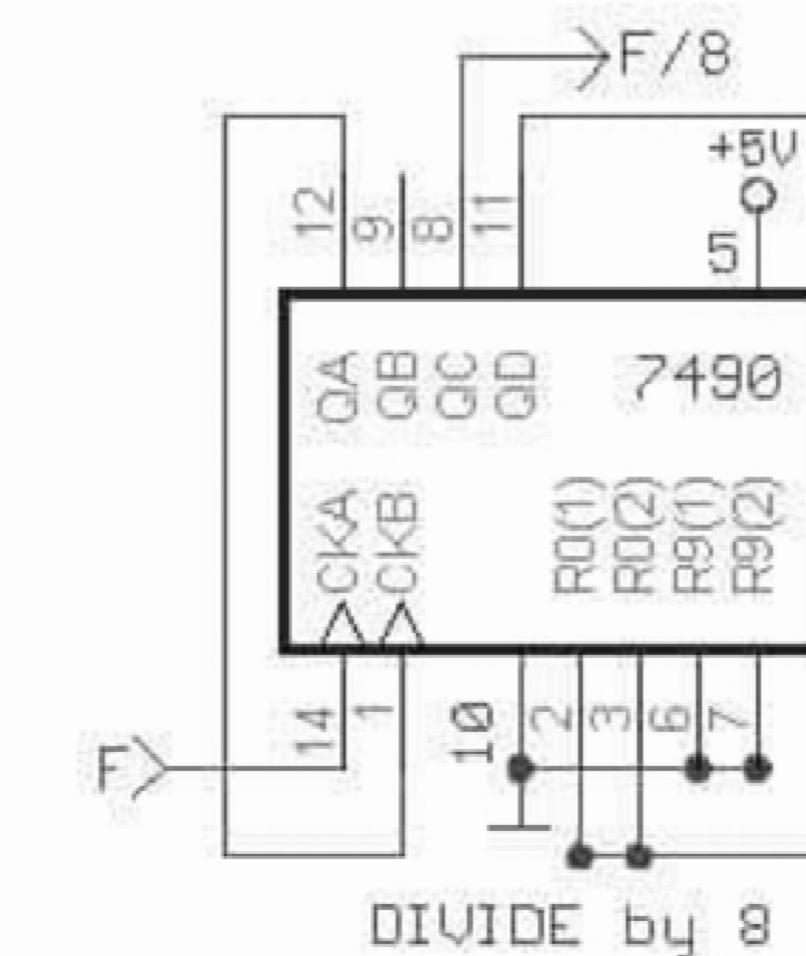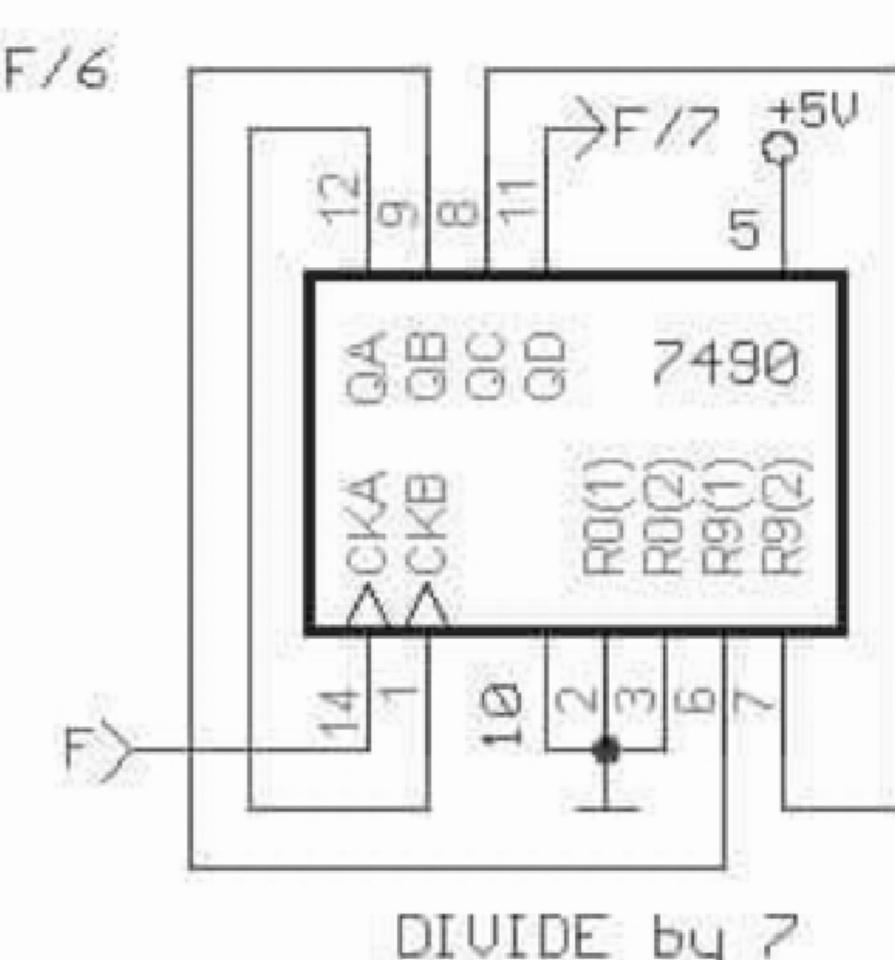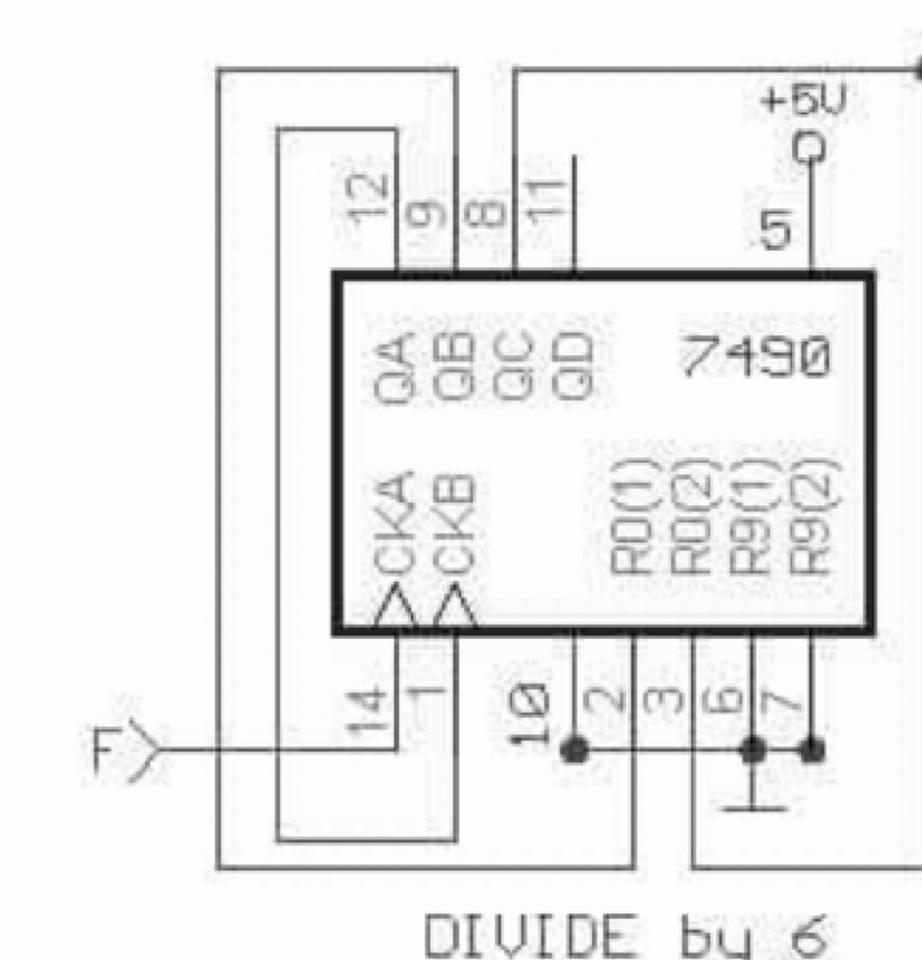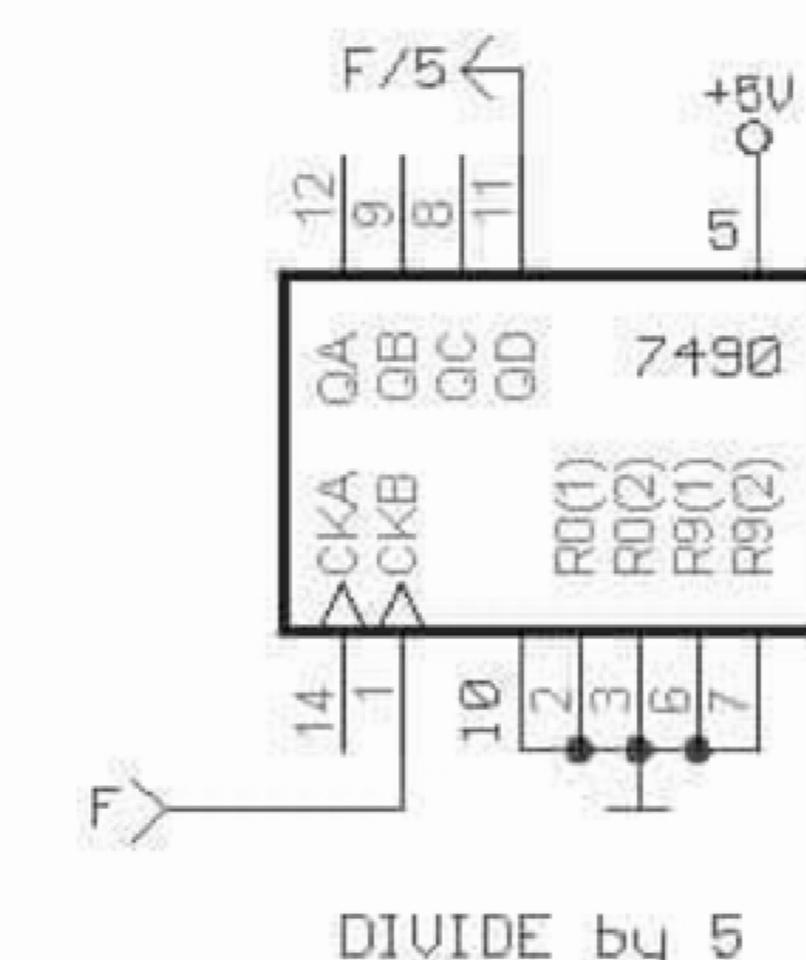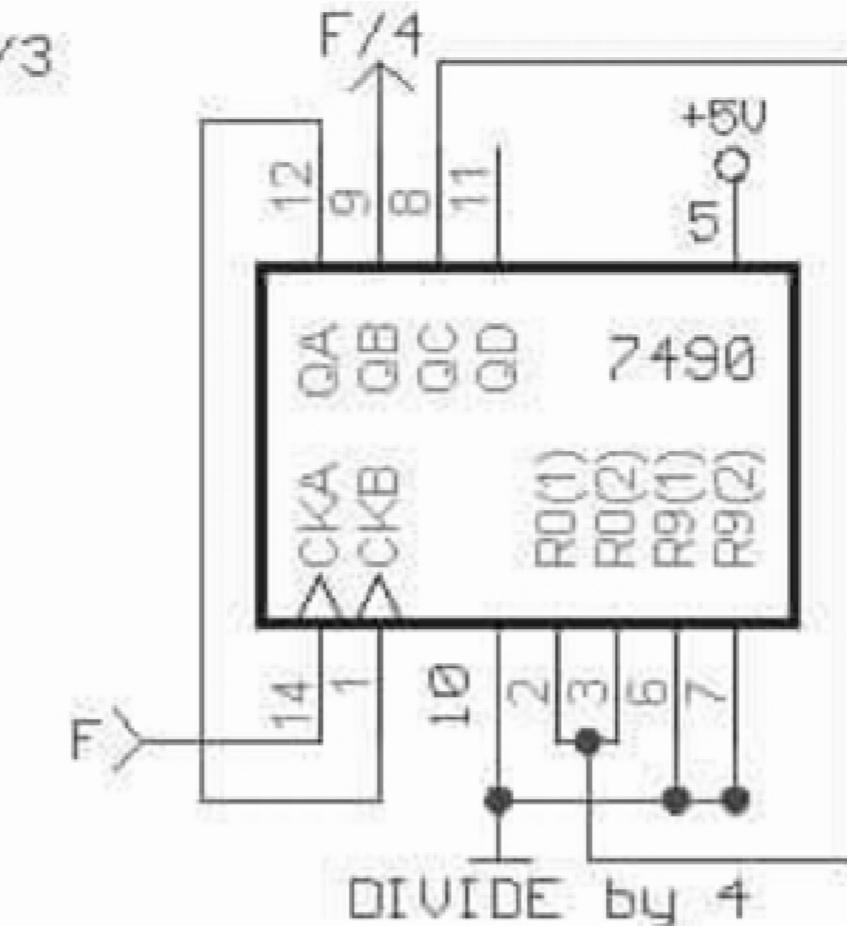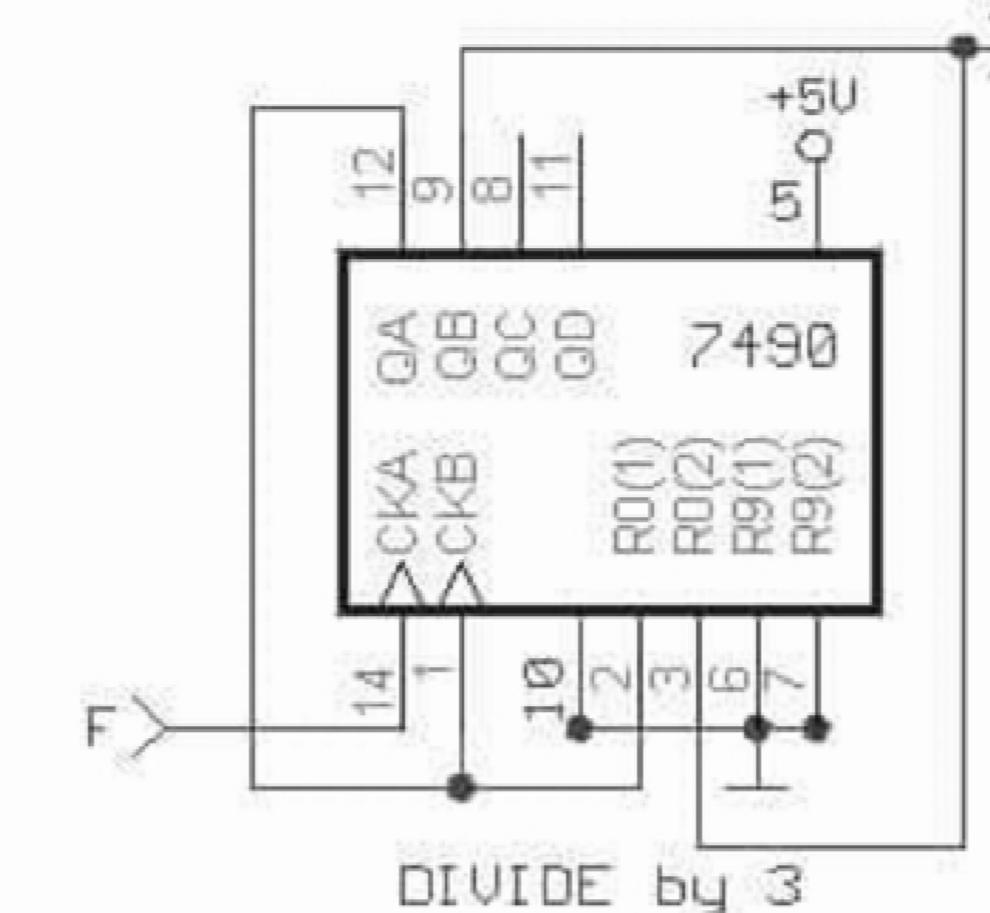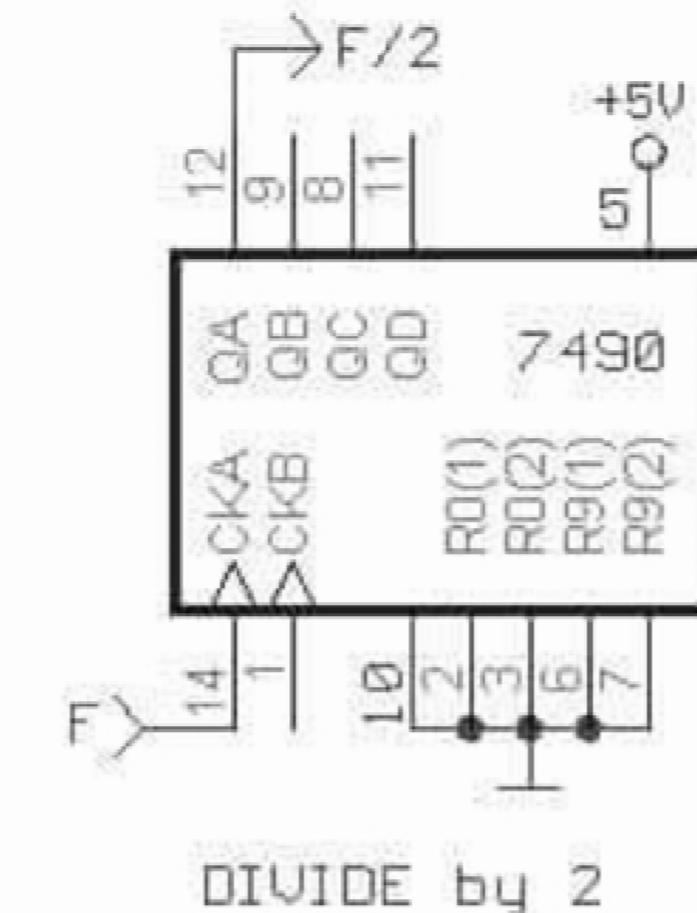

# Practical

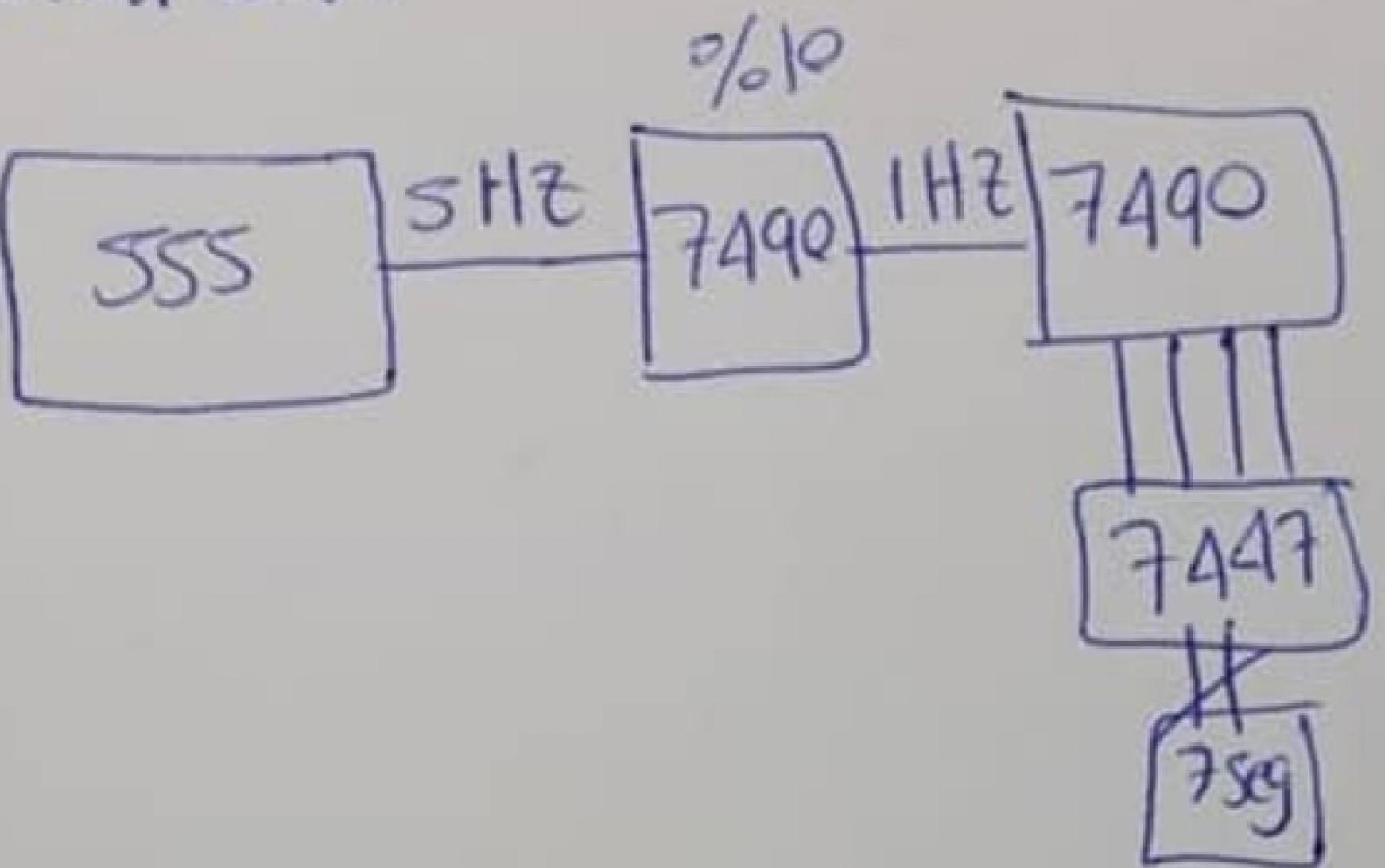


$$R_1 = 88000$$

$$R_2 = 100000$$

$$C = 1 \mu F$$


I divide  
by 5.

-  $F_{aud} = 1\text{Hz}$

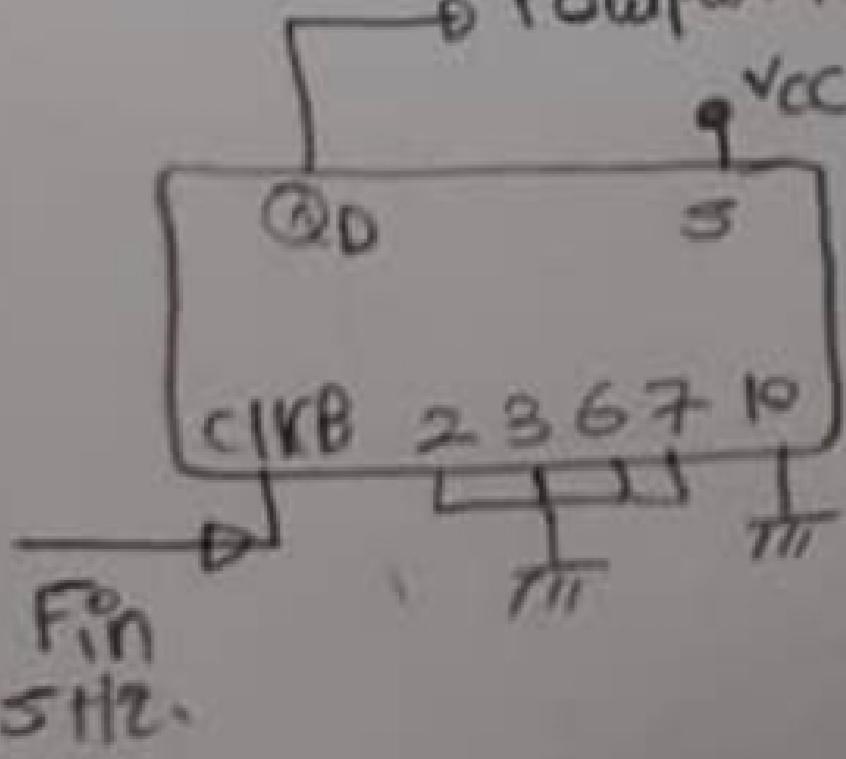

$\rightarrow$  SH $\ddot{\text{c}}$



## 2 Second Counter

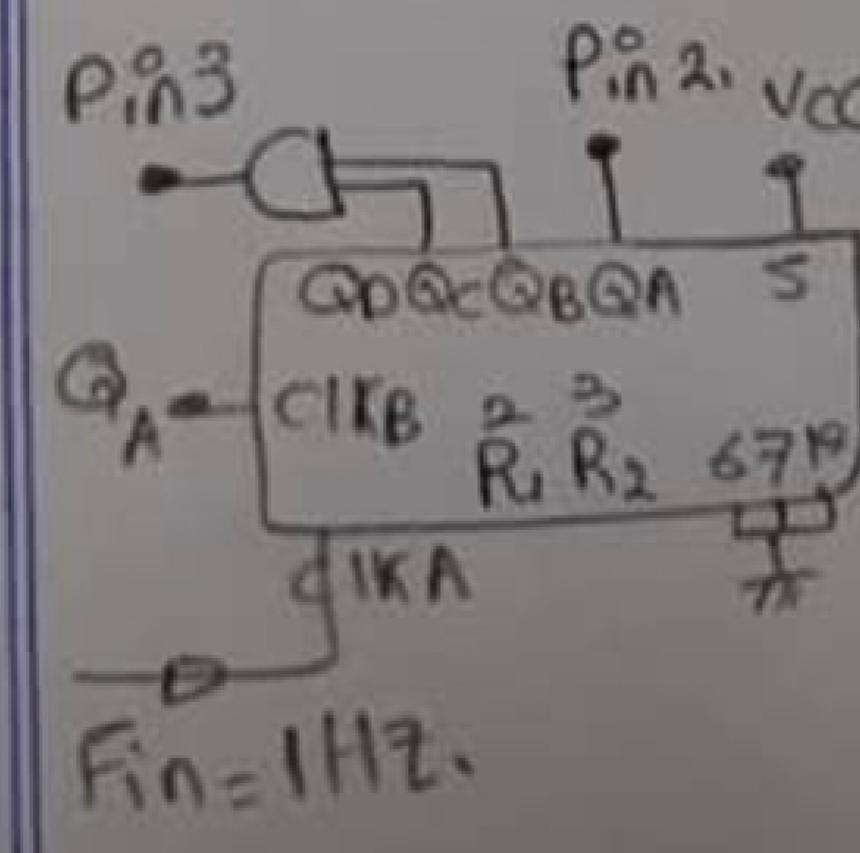

Count from 0 - 97  
for 45 sec

50
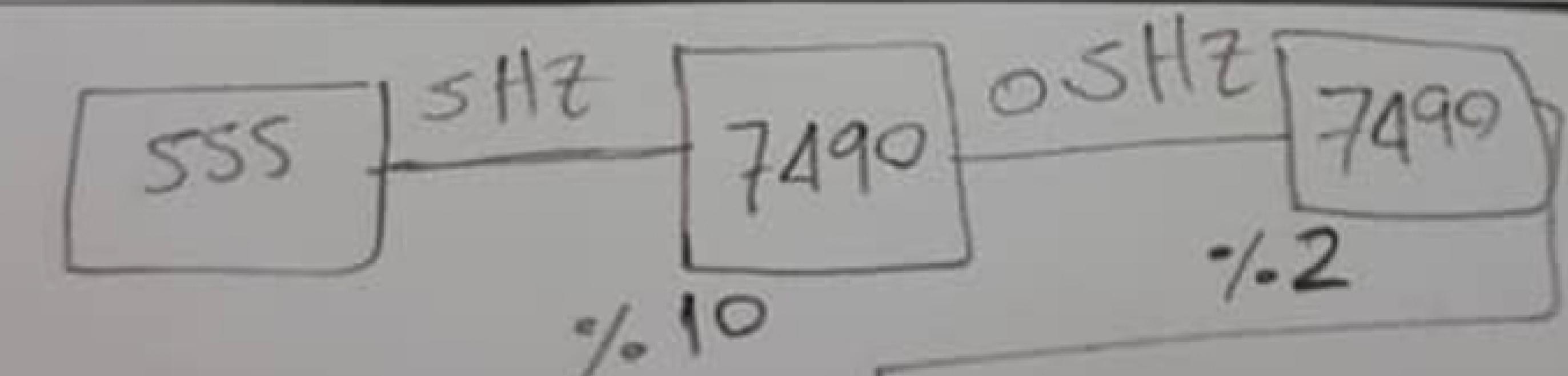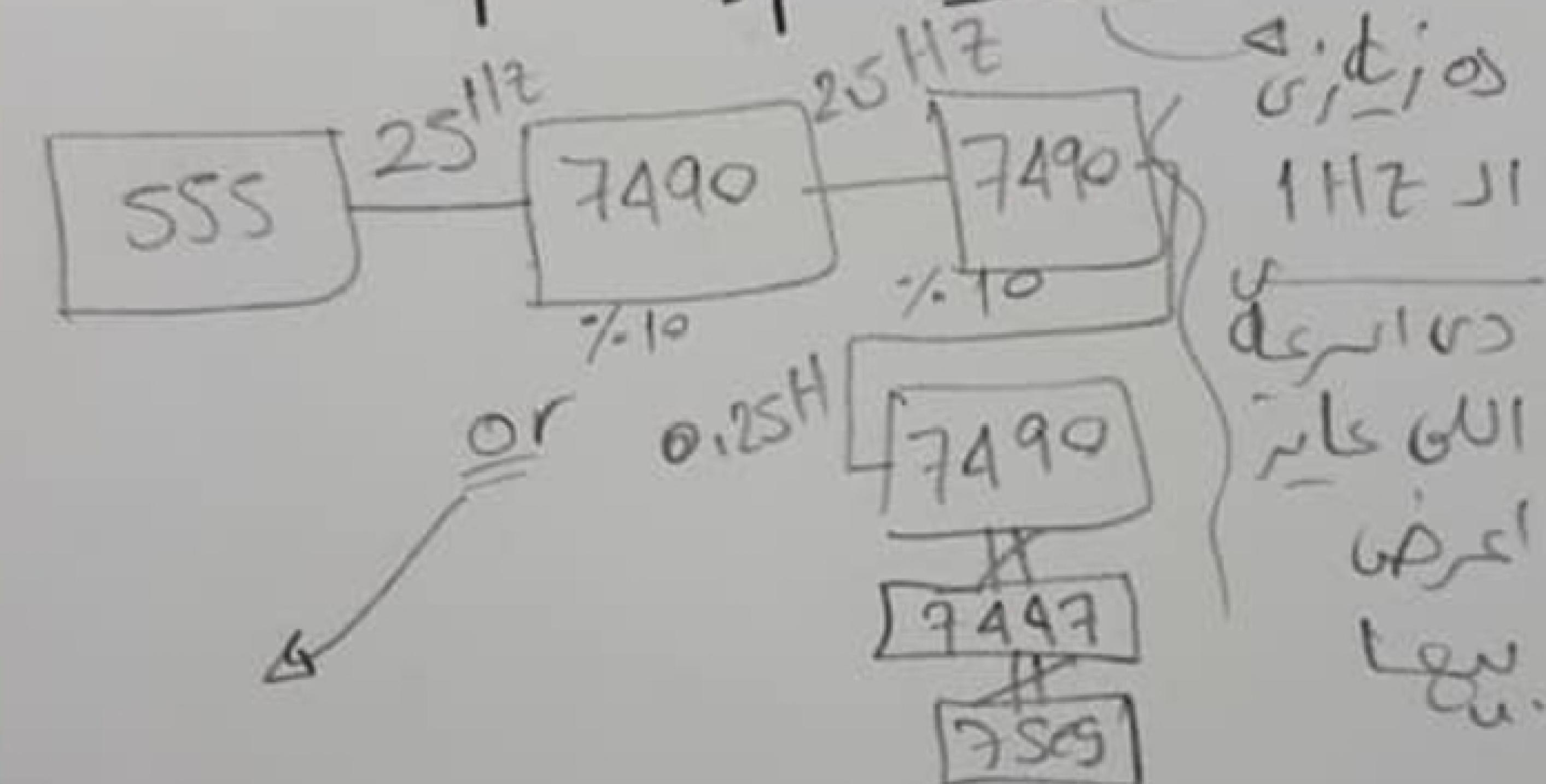
$$F = \frac{1}{T} = \frac{1}{4} = \boxed{0.25} \text{ Hz.}$$



1

✓. 10

4

丁

1

10

10



82


10. The following table summarizes the results of the study. The first column lists the variables, the second column lists the sample size, and the third column lists the estimated effect sizes.

design a circuit to produce  
Count from 0 → 7  
for 4 sec

Sol
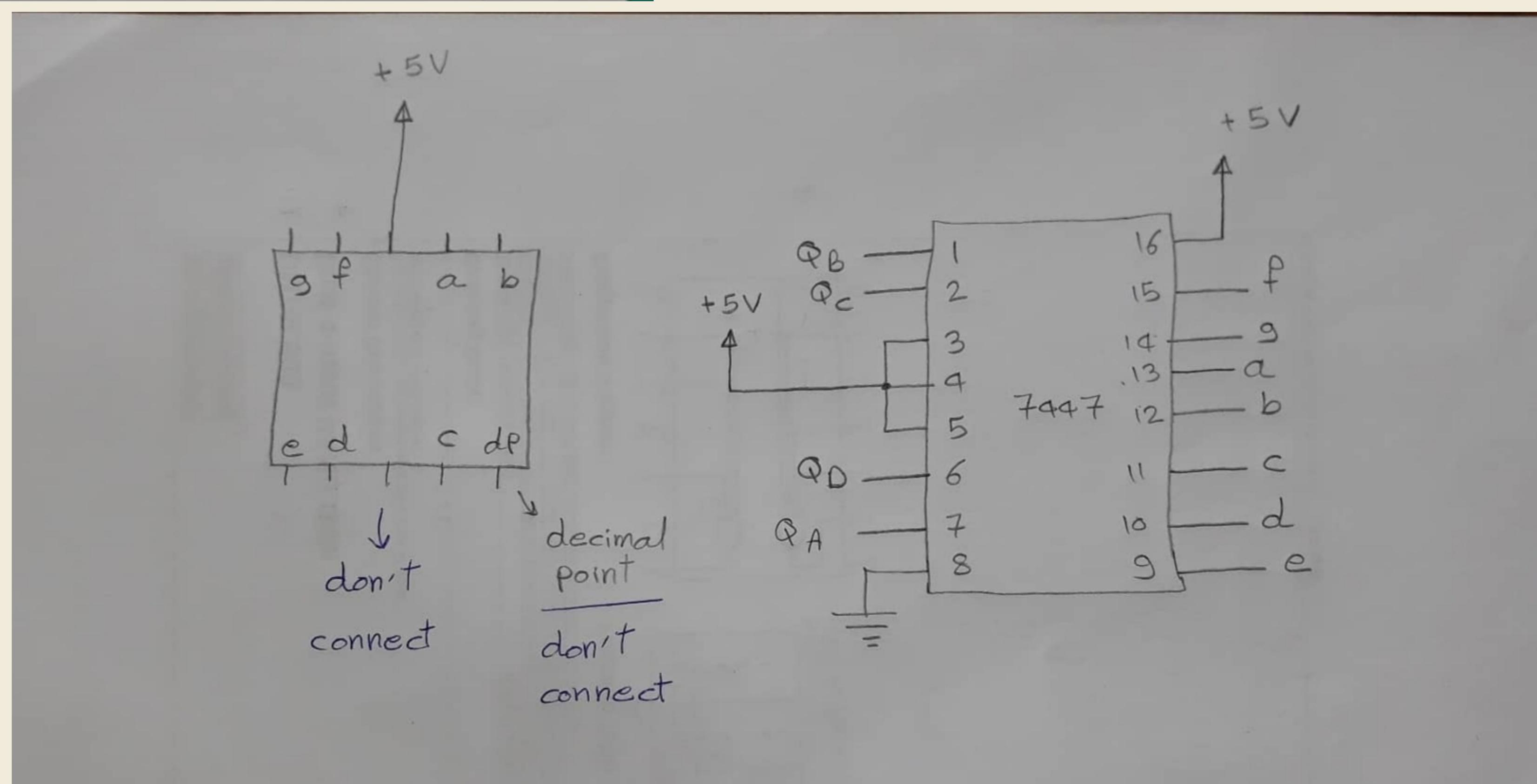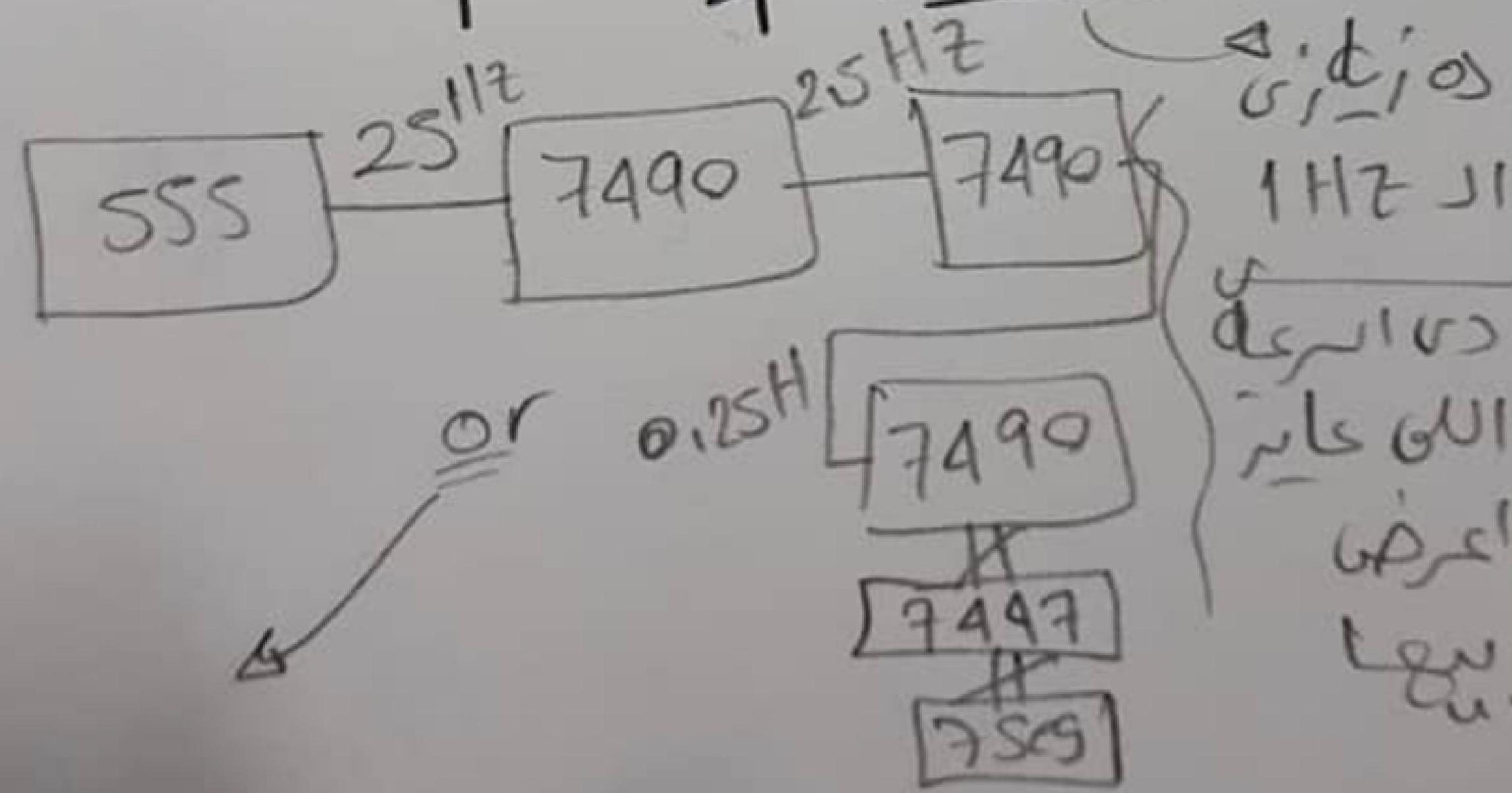
$$F = \frac{1}{T} = \frac{1}{4} = 0.25 \text{ Hz.}$$



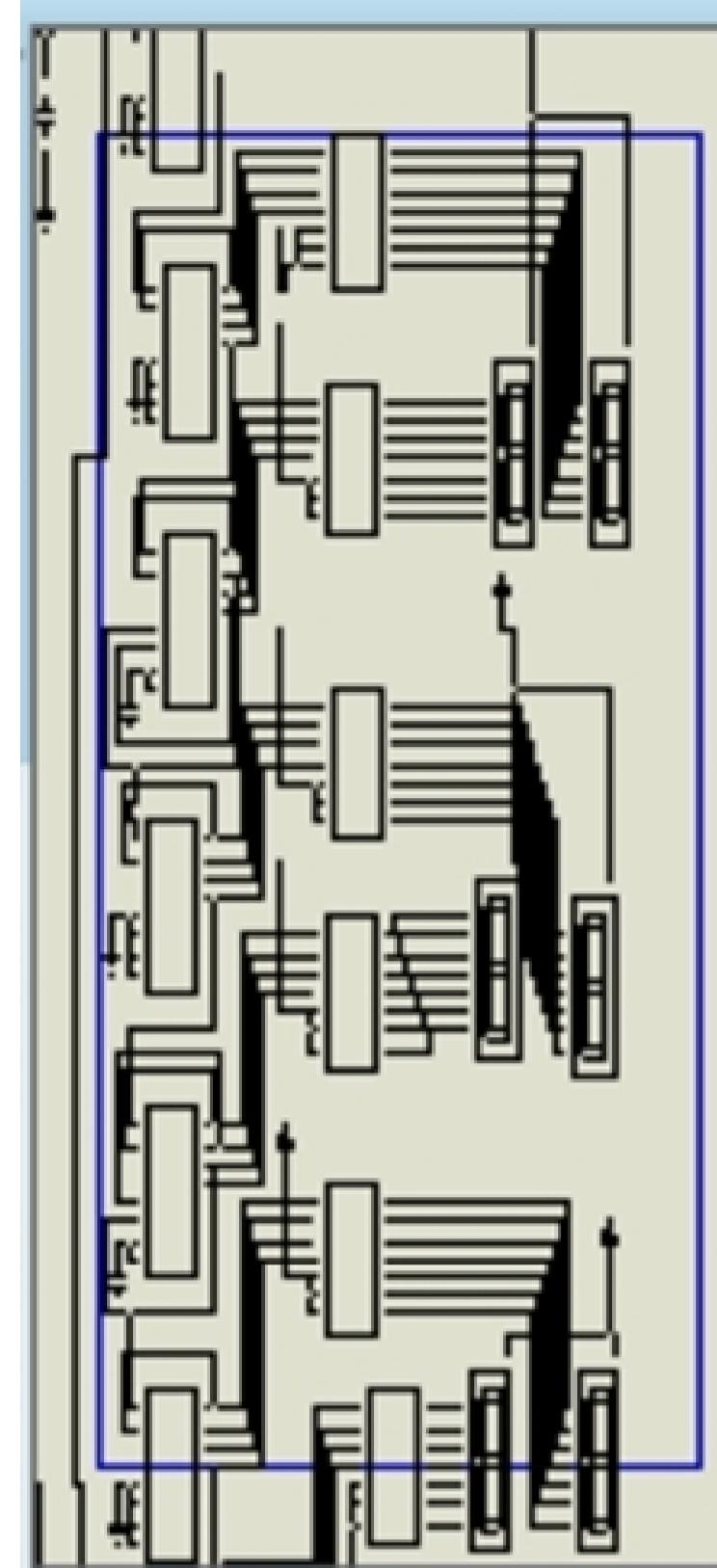

P L DEVICES

7SEG-COM-ANODE

74LS47

74LS90

555

3252W-1-101LF

3252W-1-501LF


7490

CAP

MINRES120K


POT

RES


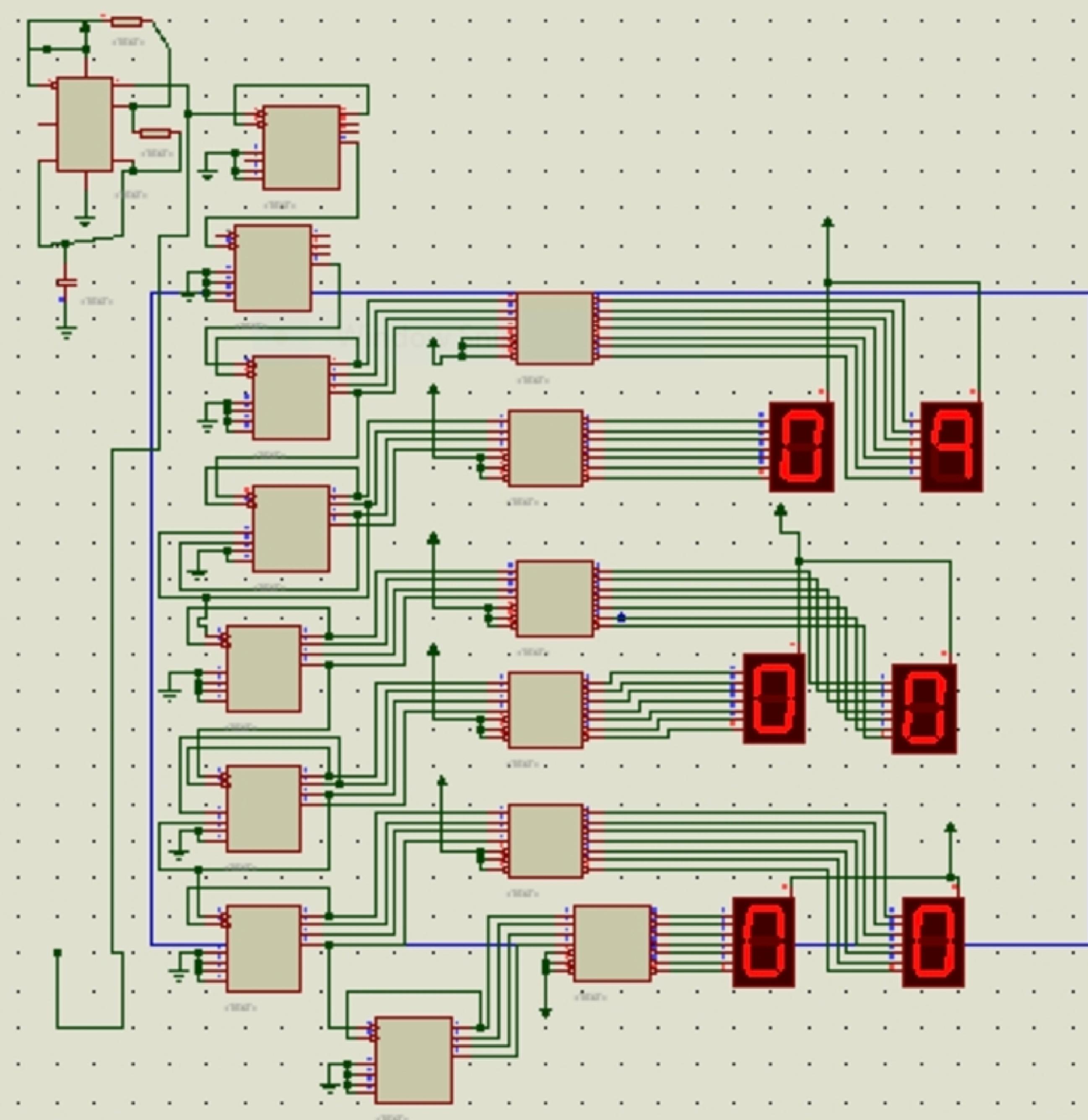


Block Diagram


$$t = \frac{1}{f}$$

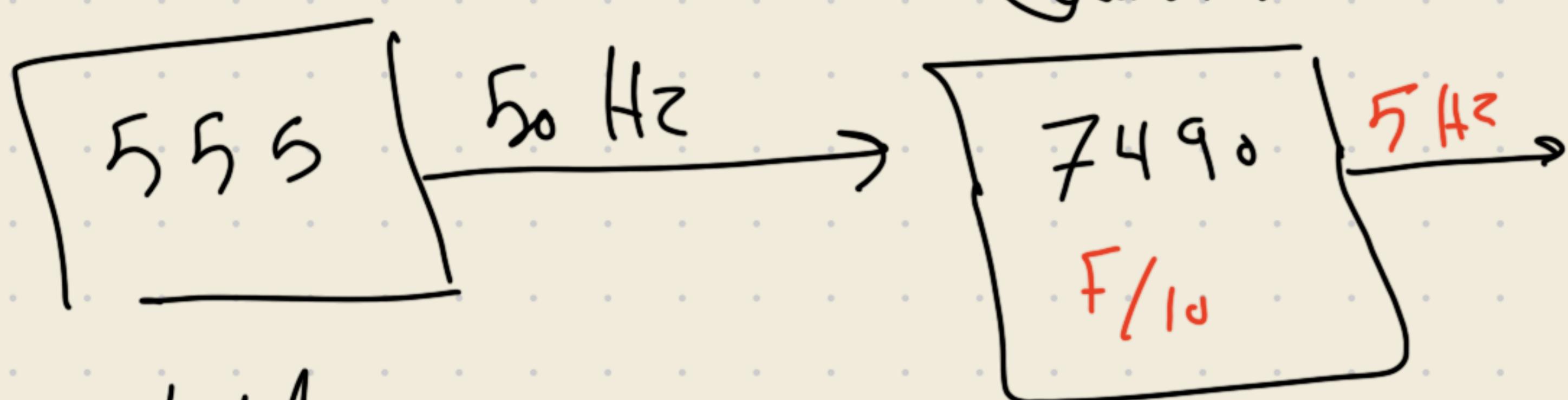



A stable  
timer

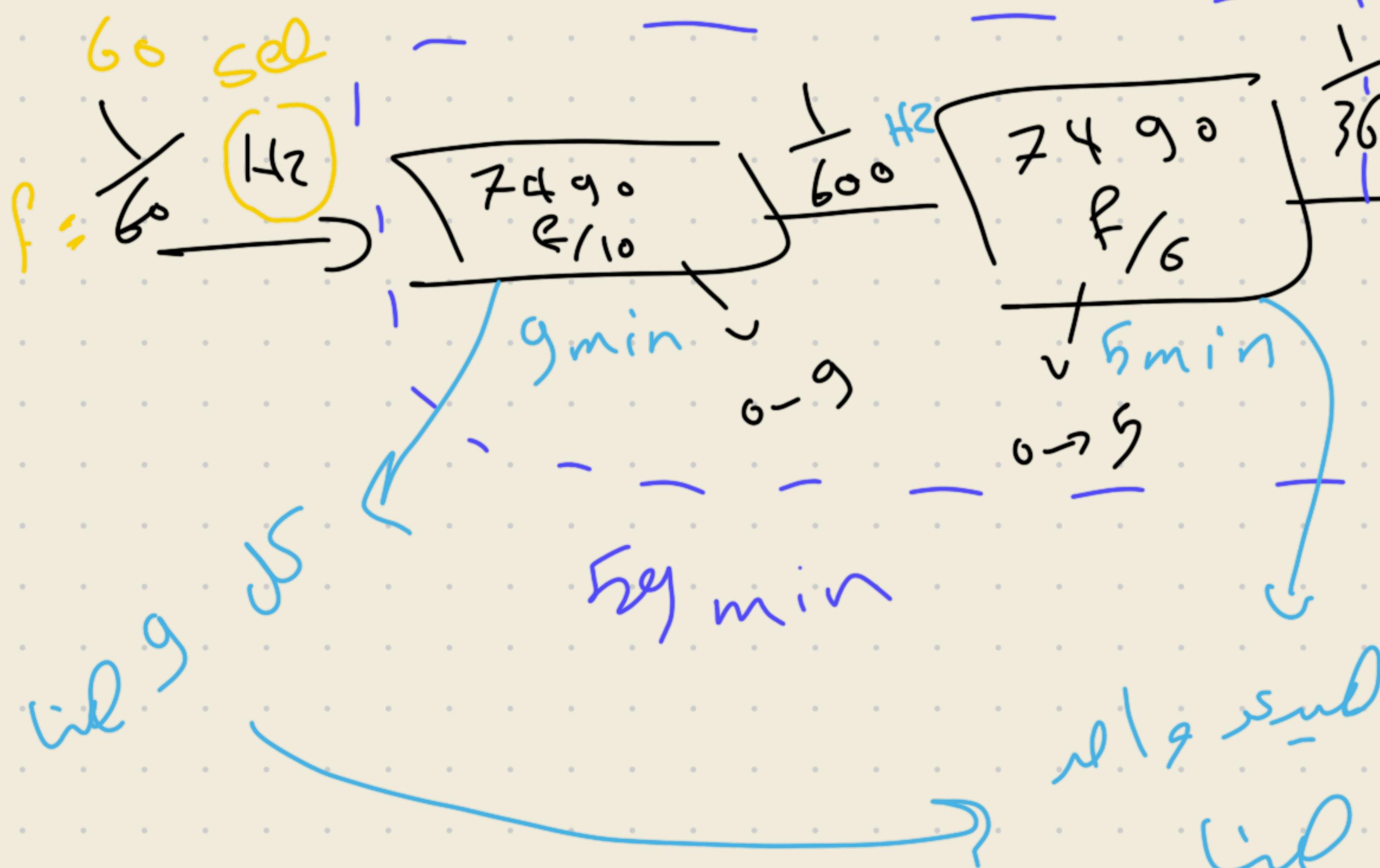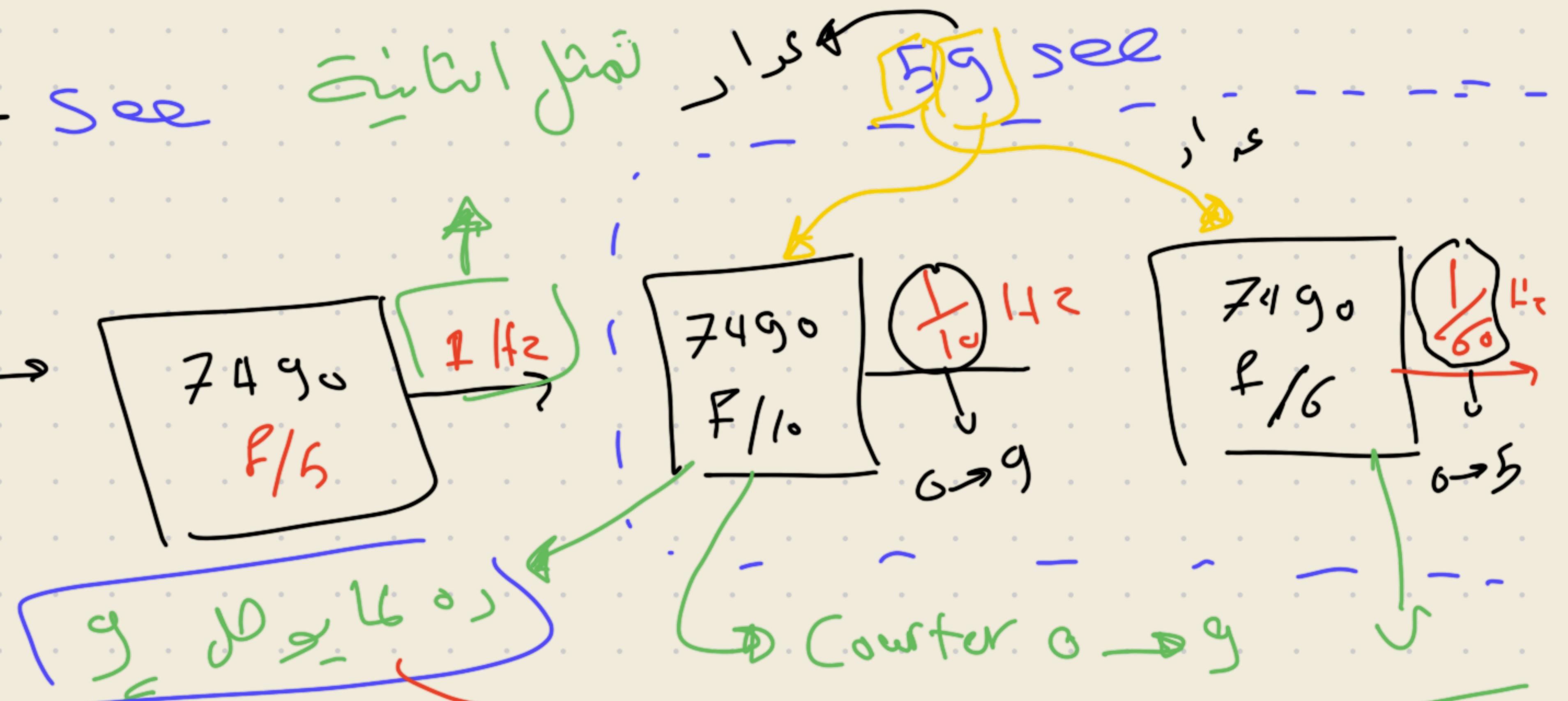

اول طلب  
تسلیم 24H  
جهات  
Reset  
inail contacts

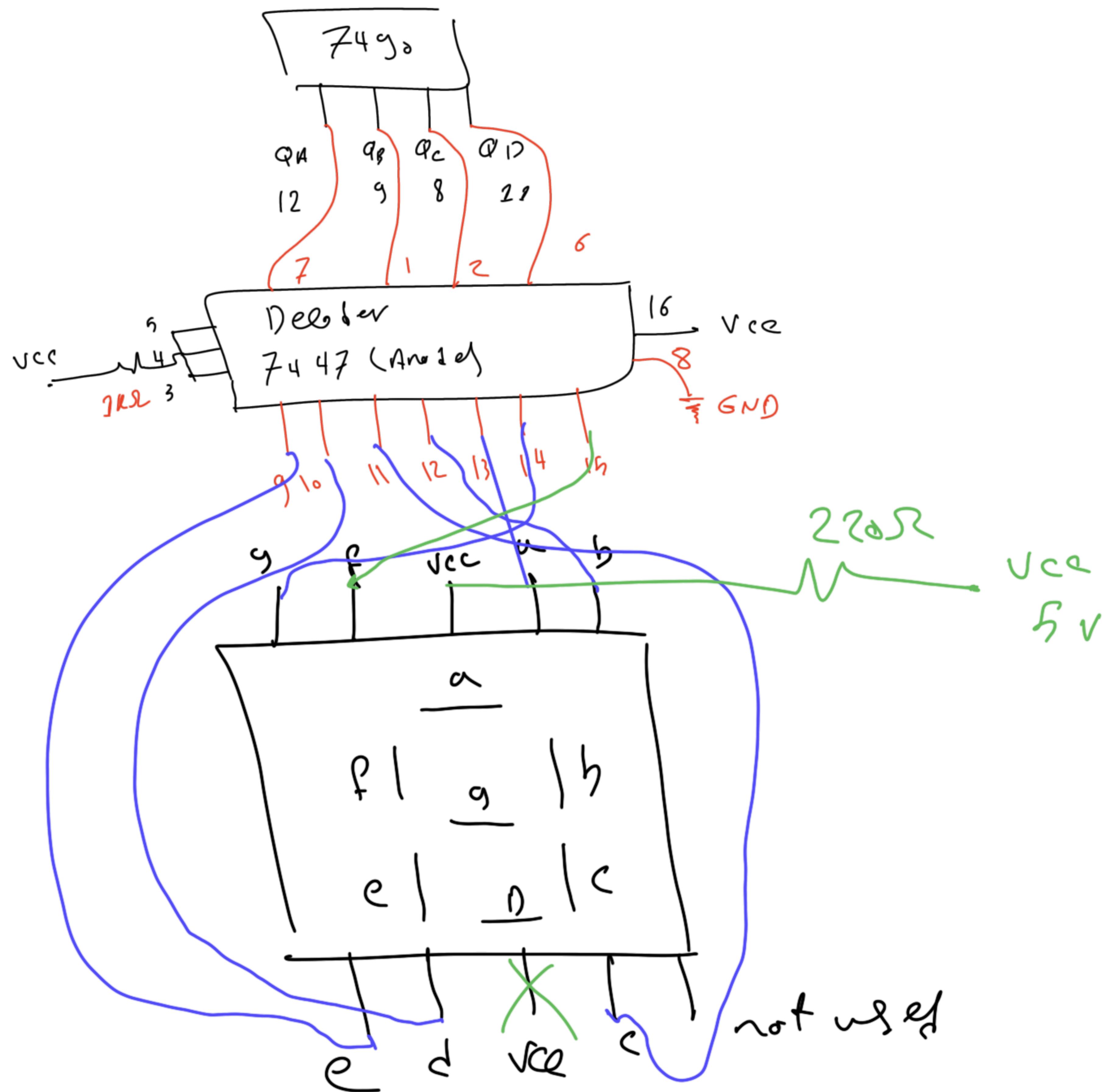

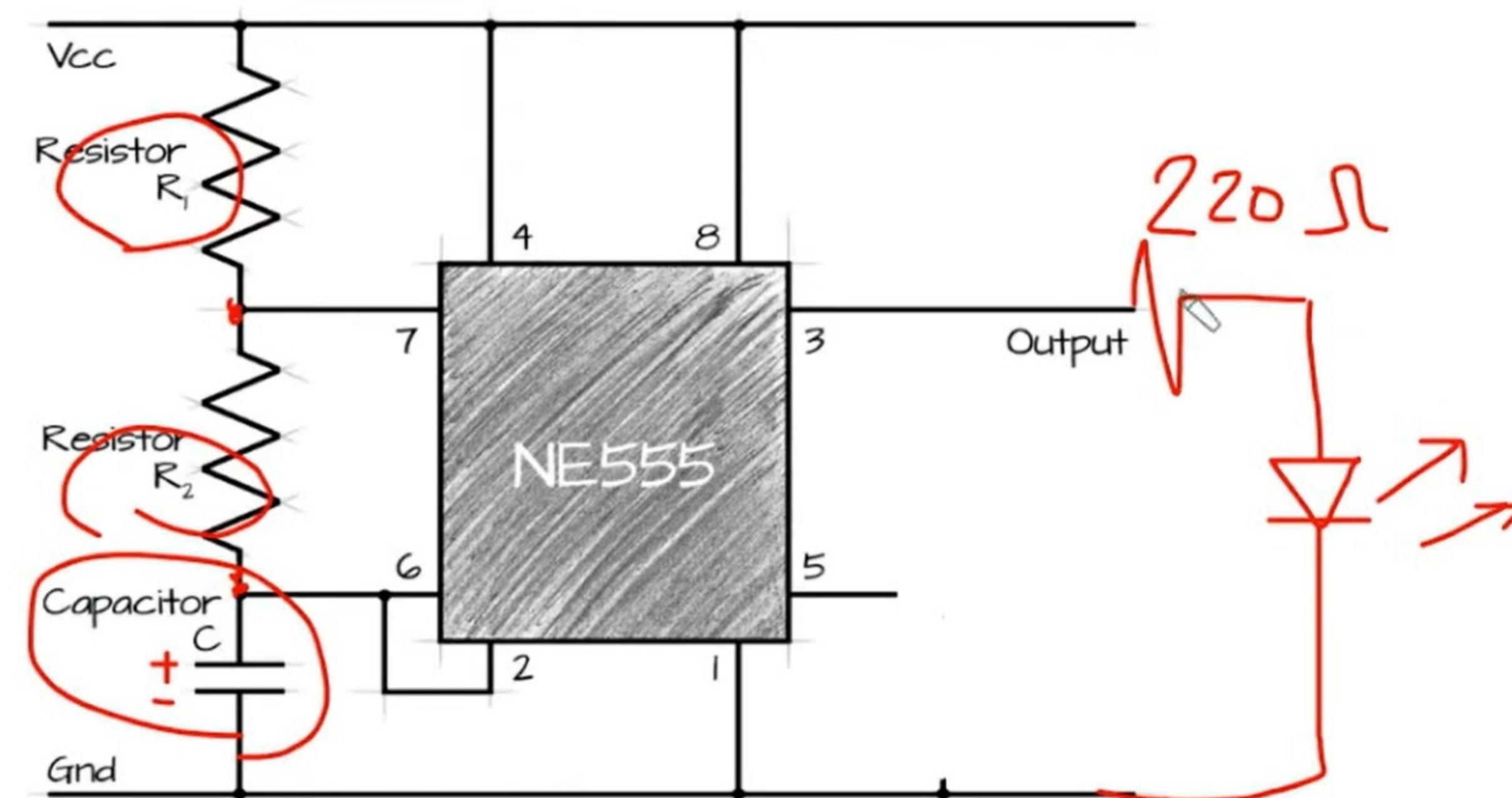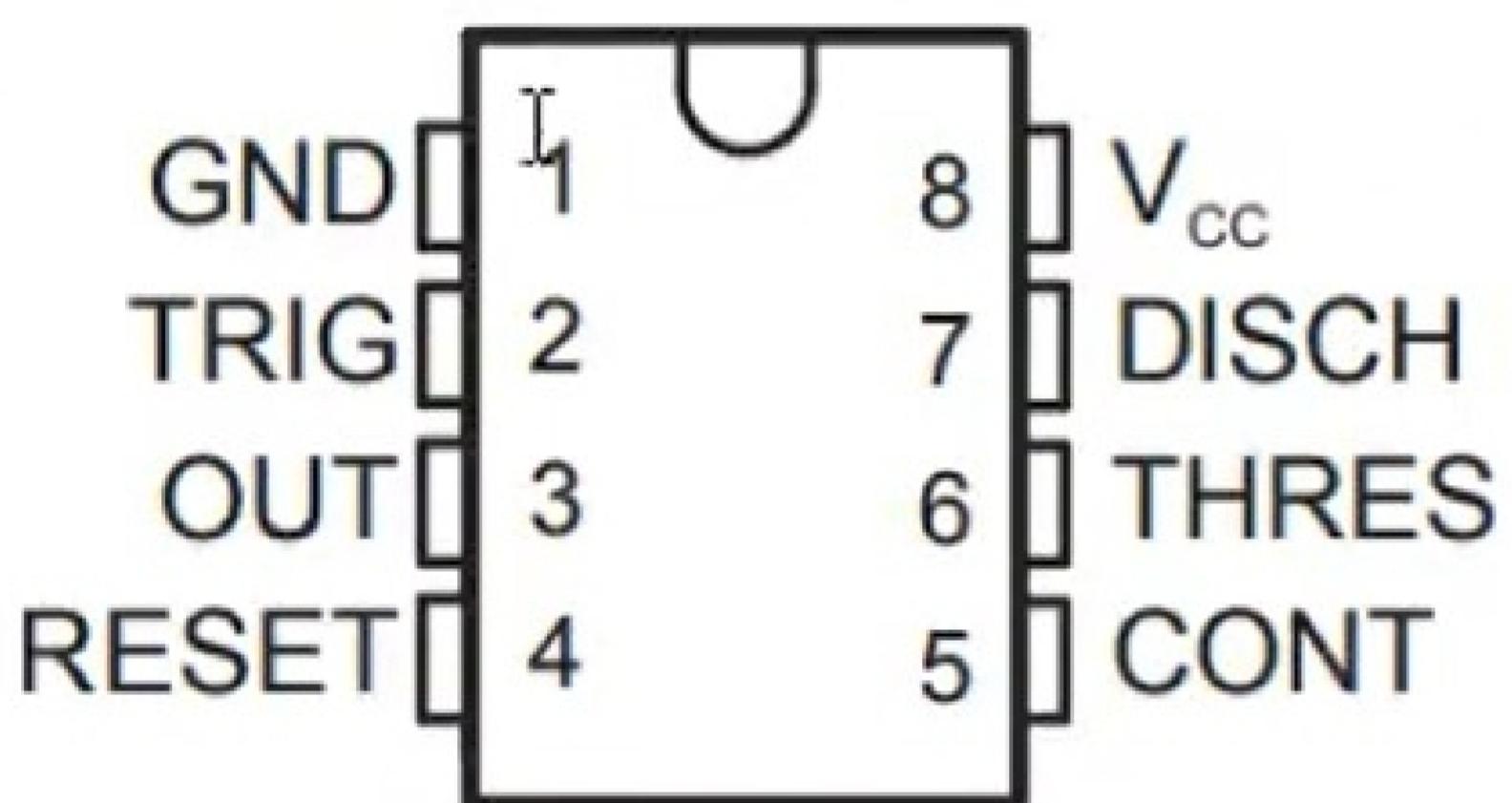**NA555...D OR P PACKAGE**  
**NE555...D, P, PS, OR PW PACKAGE**  
**SA555...D OR P PACKAGE**  
**SE555...D, JG, OR P PACKAGE**  
**(TOP VIEW)**



$$f = \frac{1.44}{(R_1 + 2R_2) C} = 50 \text{ Hz}$$

Capacitor (C)	<input type="text" value="1"/>
Resistance 1 ( $R_1$ )	<input type="text" value="500"/>
Resistance 2 ( $R_2$ )	<input type="text" value="14"/>
Frequency	<input type="text" value="50.632"/> H <sub>2</sub>
Period (T)	<input type="text" value="19.750"/>
Duty Cycle	<input type="text" value="50.88"/>
Time High (T <sub>1</sub> )	<input type="text" value="10.049"/>

Capacitor (C)	<input type="text" value="47"/>
Resistance 1 ( $R_1$ )	<input type="text" value="10"/>
Resistance 2 ( $R_2$ )	<input type="text" value="10"/>
Frequency	<input type="text" value="1.023"/>
Period (T)	<input type="text" value="977.130"/>
Duty Cycle	<input type="text" value="66.67"/>
Time High (T <sub>1</sub> )	<input type="text" value="651.420"/>

Red arrows pointing to the second row of each table.

